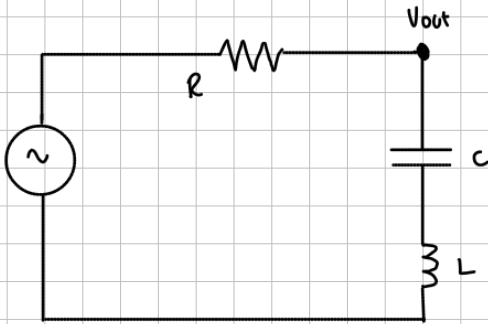




$$R = 100 \text{ K } \Omega$$

$$C = 3.18 \text{ nF}$$

$$L = 31.83 \text{ mH}$$

$$Z_C = \frac{1}{sC} = \frac{314465.48}{s}$$

$$Z_L = 31.83 s$$

$$V_{out} = V_{in} \cdot \frac{Z_C + Z_L}{R + Z_C + Z_L}$$

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{Z_C + Z_L}{R + Z_C + Z_L} = \frac{\frac{1}{sC} + sL}{R + \frac{1}{sC} + sL}$$

$$\frac{\frac{1}{sC} + sL}{R + \frac{1}{sC} + sL} \cdot \frac{sC}{sC} = \frac{1 + s^2 LC}{s^2 LC + sRC + 1}$$

Para passar a forma canônica

$$\frac{1 + s^2 LC}{s^2 LC + sRC + 1} \cdot \frac{\frac{1}{LC}}{\frac{1}{LC}} \Rightarrow \frac{s^2 + \frac{1}{LC}}{s^2 + s \frac{R}{L} + \frac{1}{LC}} \quad \text{que é } \frac{s^2 + \omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

$$L \cdot C = 31.83 \cdot 10^{-3} \text{ H} \cdot 3.18 \cdot 10^{-6} \text{ F} = 1.0122 \cdot 10^{-7}$$

$$H(s) = \frac{s^2 + \frac{1}{1.0122 \cdot 10^{-7}}}{s^2 + s \frac{100}{31.83 \cdot 10^{-3}} + \frac{1}{1.0122 \cdot 10^{-7}}}$$

Reemplazamos por "jw"

$$H(j\omega) = \frac{-\omega^2 + \frac{1}{1.0122 \cdot 10^{-7}}}{-\omega^2 + j\omega \frac{100}{31.83 \cdot 10^{-3}} + \frac{1}{1.0122 \cdot 10^{-7}}}$$

separamos parte real e imaginaria


$$\frac{-\omega^2 + \frac{1}{1.0122 \cdot 10^{-7}}}{-\omega^2 + j\omega \frac{100}{31.83 \cdot 10^{-3}} + \frac{1}{1.0122 \cdot 10^{-7}}} \Rightarrow \frac{\overset{A}{\omega_0^2 - \omega^2}}{\omega_0^2 - \omega^2 + j\omega \frac{R}{L}} \Rightarrow \frac{A}{A + jB}$$

$$\frac{A}{A + jB} \cdot \frac{A - jB}{A - jB} = \frac{A^2 - jAB}{A^2 - jAB + jAB + B^2} = \frac{A^2}{A^2 + B^2} - j \frac{AB}{A^2 + B^2}$$

$$Re = \frac{(\omega_0^2 - \omega^2)^2}{(\omega_0^2 - \omega^2)^2 + \left(\omega \frac{R}{L}\right)^2} \quad Im = \frac{(\omega_0^2 - \omega^2) \cdot \omega \frac{R}{L}}{(\omega_0^2 - \omega^2)^2 + \left(\omega \frac{R}{L}\right)^2}$$

diagrama polar

ω	Re	Im
0	1	0
2π	0,2	-0,4
$\hat{\pi}$	0,5	-0,5
$100 \cdot 10^3 \cdot 2\pi$	0,03	0,2
$100 \cdot 10^4 \cdot 2\pi$	0,8	0,4
$500 \cdot 10^3 \cdot 2\pi$	0,5	0,5
$500 \cdot 2\pi$	≈ 0	≈ 0
$0,25 \cdot 2\pi$	0,4	-0,4

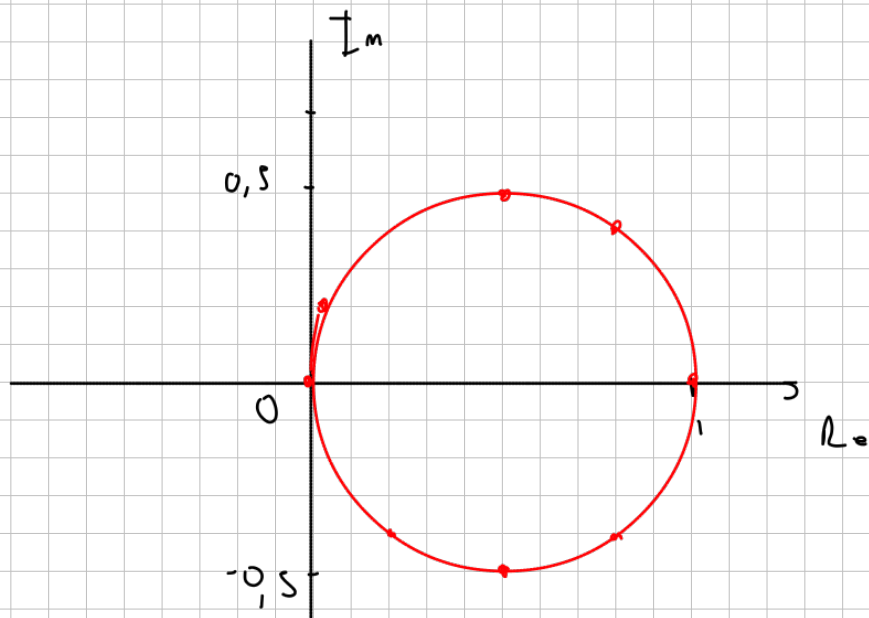

$$H(s) = \frac{s^2 + \frac{1}{1,0122 \cdot 10^{-7}}}{s^2 + \frac{s \cdot 10^5}{31,83 \cdot 10^{-3}} + \frac{1}{1,0122 \cdot 10^{-7}}}$$

por Bode

$$\text{Num} = \frac{1}{1,0122 \cdot 10^{-7}} \left(\frac{s^2}{\frac{1}{1,0122 \cdot 10^{-7}}} + 1 \right)$$

$$* = 9,879 \cdot 10^6 = p_1 \cdot p_2$$

$$\text{den} = (s + 3,144) \cdot (s + 3,142 \cdot 10^6)$$

$$\frac{3,144}{p_1} \cdot \left(\frac{s}{3,144} + 1 \right) \cdot \frac{3,142 \cdot 10^6}{p_2} \cdot \left(\frac{s}{3,142 \cdot 10^6} + 1 \right)$$

$$H(s) = \frac{\left(\frac{s^2}{9,879 \cdot 10^6} + 1 \right)}{\left(\frac{s}{3,144} + 1 \right) \cdot \left(\frac{s}{3,142 \cdot 10^6} + 1 \right)}$$

$$\text{cte} = 1$$

$$\text{Cero doble en } \frac{\sqrt{9,879 \cdot 10^6}}{2\pi} = 500 \text{ Hz}$$

$$\text{Polo simple en } \frac{3,144}{2\pi} = 0,5 \text{ Hz}$$

$$\text{Polo simple en } \frac{3,142 \cdot 10^6}{2\pi} \approx 500 \text{ KHz}$$

