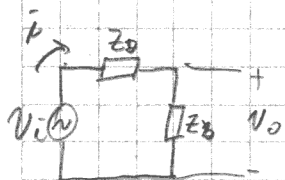



Analisis como cadena de divisores resistivos



$$V_o = \bar{i} \cdot Z_b$$

$$V_o = \frac{V_i}{Z_a + Z_b} Z_b$$

Desarrollamos a Laplace (sin C.I)

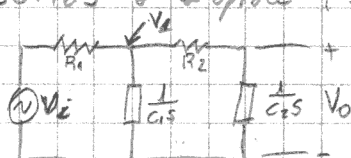

$$V_1 = \frac{V_i}{R_1 + \frac{1}{C_1 s}} \cdot \frac{1}{C_1 s}$$

$$V_o = \frac{V_1}{R_2 + \frac{1}{C_2 s}} \cdot \frac{1}{C_2 s}$$

Forma Polar: $s \rightarrow j\omega$

$$H(j\omega) = \frac{1}{R_1 R_2 C_1 C_2} \frac{1}{\left(j\omega + \frac{1}{R_1 C_1}\right) \left(j\omega + \frac{1}{R_2 C_2}\right)}$$

$$V_o = V_i \cdot \frac{1}{\left(R_1 + \frac{1}{C_1 s}\right) C_1 s} \cdot \frac{1}{\left(R_2 + \frac{1}{C_2 s}\right) C_2 s}$$

$$= \frac{1}{R_1 R_2 C_1 C_2} \frac{1}{-\omega^2 + \frac{j\omega}{R_2 C_2} + \frac{j\omega}{R_1 C_1} + \frac{1}{R_1 C_1 R_2 C_2}}$$

$$\frac{V_o}{V_i} = H(s) = \frac{1}{R_1 C_1 s + 1} \cdot \frac{1}{R_2 C_2 s + 1}$$

$$= \frac{1}{(1 - R_1 R_2 C_1 C_2 \omega^2) + j\omega(R_1 C_1 + R_2 C_2)}$$

$$H(s) = \frac{1}{R_1 C_1 R_2 C_2} \frac{1}{\left(s + \frac{1}{R_1 C_1}\right) \left(s + \frac{1}{R_2 C_2}\right)}$$

Multiplicar por el conj.

$$= \frac{1 - R_1 R_2 C_1 C_2 \omega^2 - j\omega(R_1 C_1 + R_2 C_2)}{(1 - R_1 R_2 C_1 C_2 \omega^2)^2 + \omega^2(R_1 C_1 + R_2 C_2)^2}$$

$$H(s) = \frac{18,2967 \times 10^9}{(s + 109890,1094)(s + 166500,1665)}$$

$$\operatorname{Re}\{H(j\omega)\} = \frac{1 - R_1 R_2 C_1 C_2 \omega^2}{(1 - R_1 R_2 C_1 C_2 \omega^2)^2 + \omega^2(R_1 C_1 + R_2 C_2)^2}$$

Ceros $\rightarrow$ NO

$$\operatorname{Re}\{H(j\omega)\} = \frac{1 - \omega^2 \cdot 54,65 \times 10^{-12}}{(1 - \omega^2 \cdot 54,65 \times 10^{-12})^2 + \omega^2(9,1 \times 10^{-6} + 6 \times 10^{-6})^2}$$




Polos $\rightarrow \omega = 109890,1094 \approx 10^5$

$$\hookrightarrow \omega = 166500,1665 \approx 1,6 \times 10^5$$

$$\operatorname{Im}\{H(j\omega)\} = \frac{-\omega(R_1 C_1 + R_2 C_2)}{(1 - R_1 R_2 C_1 C_2 \omega^2)^2 + \omega^2(R_1 C_1 + R_2 C_2)^2}$$

$$K_{fe} = -10,25 \times 10^{-6} \text{ dB} \approx 0 \text{ dB}$$
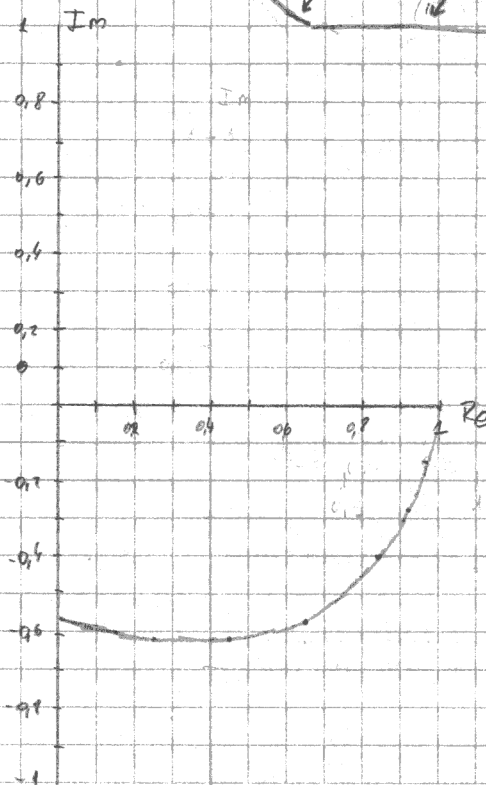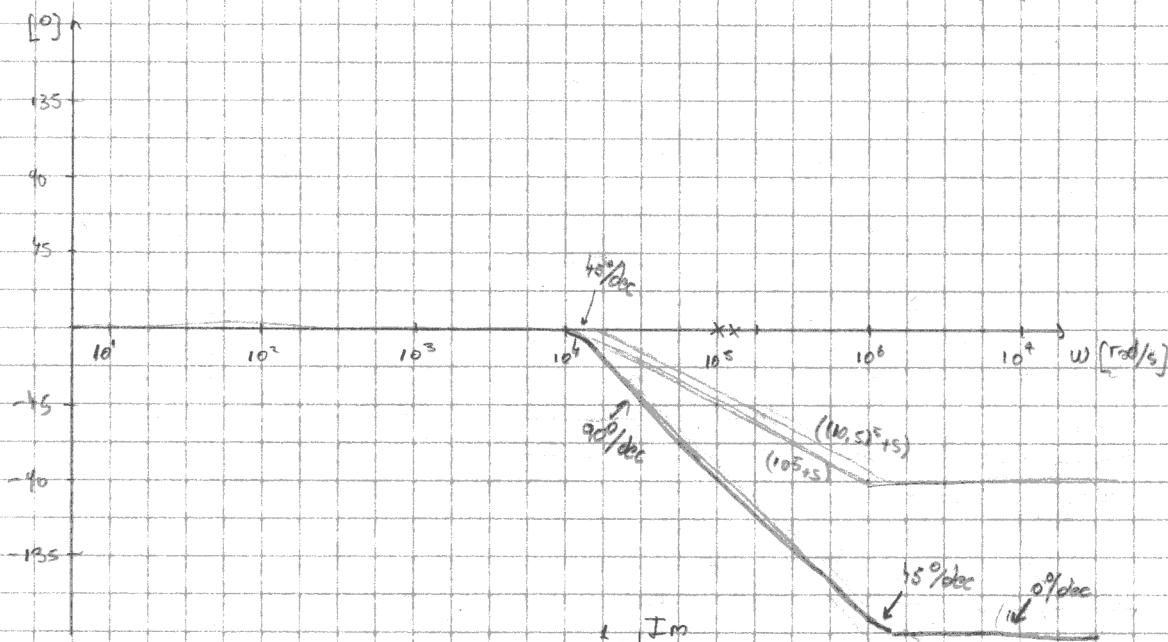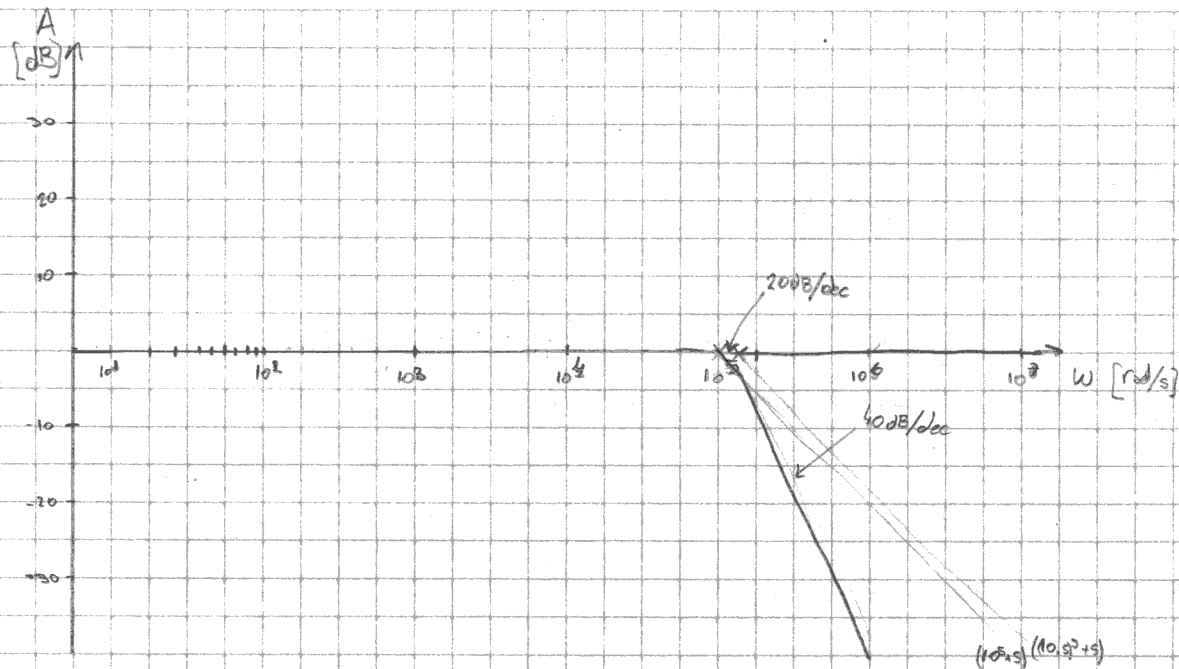
$$\operatorname{Im}\{H(j\omega)\} = \frac{-\omega(9,1 \times 10^{-6} + 6 \times 10^{-6})}{(1 - \omega^2 \cdot 54,65 \times 10^{-12})^2 + \omega^2(9,1 \times 10^{-6} + 6 \times 10^{-6})^2}$$



w	$\text{Re}\{H\}$	$\text{Im}\{H\}$
0	1	0
1	0.99	0.01
10^4	0.98	-0.14
2×10^4	0.43	-0.28
3×10^4	0.85	-0.4
5×10^4	0.65	-0.37
7×10^4	0.44	-0.63
9×10^4	0.25	-0.62
10^5	0.18	-0.6