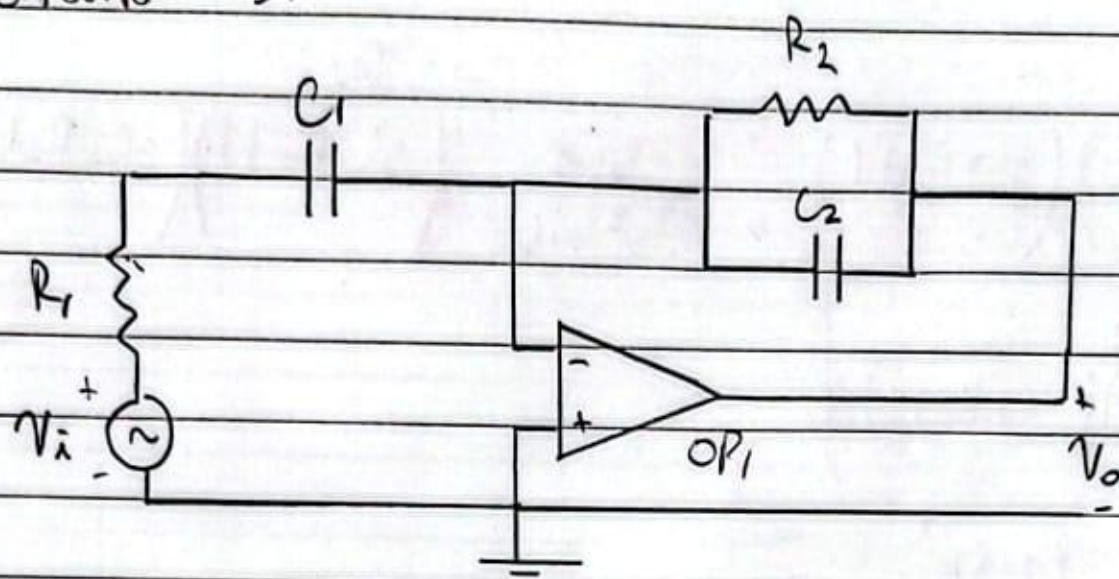


Circuito 3:





$$R_1 = 20 \text{ k}\Omega$$

$$R_2 = 400 \text{ k}\Omega$$

$$C_1 = 1,25 \mu\text{F}$$

$$C_2 = 15,625 \text{ nF}$$

$$A_V = 1 \times 10^6$$

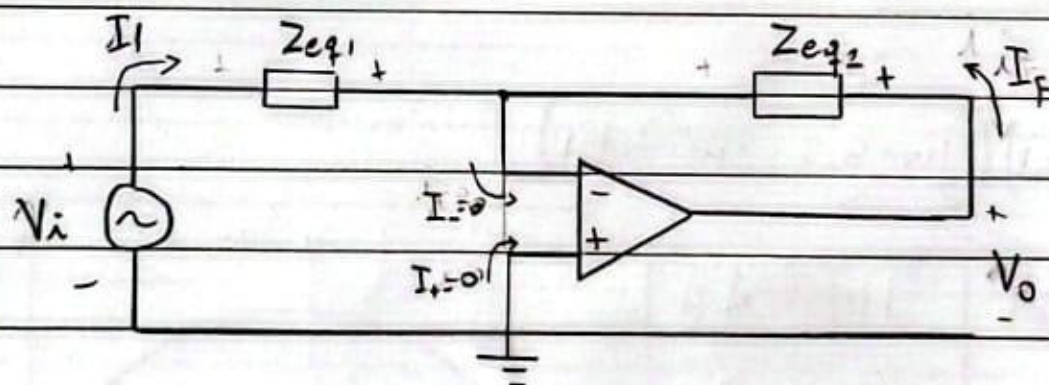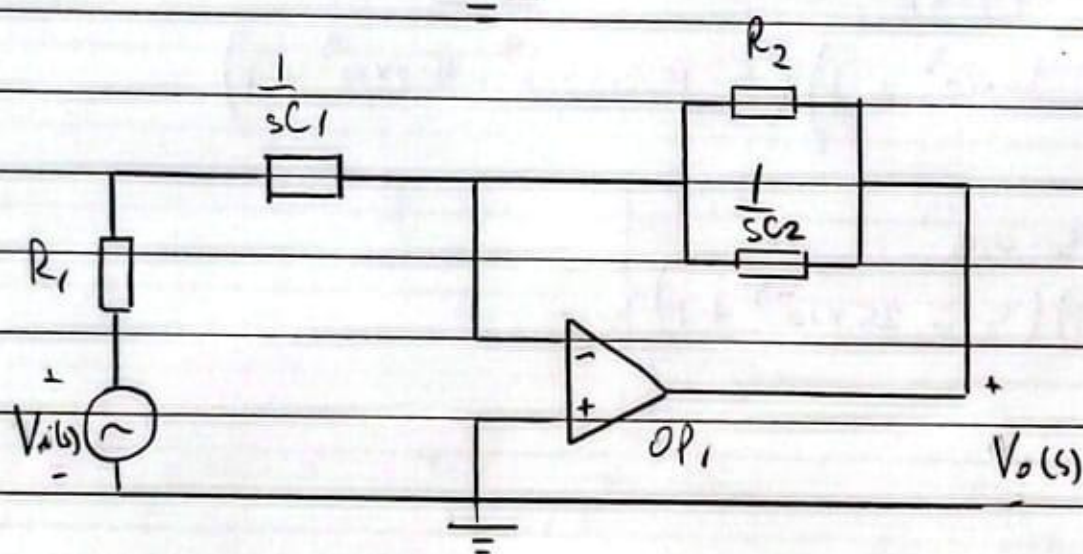

$$Z_{eq1} = R_1 + \frac{1}{sC_1}$$

$$Z_{eq2} = R_2 \parallel \frac{1}{sC_2}$$

Considerando que $V_d = V_+ - V_- = 0$, y $V_+ = 0$, por lo tanto $V_- = 0$ (tierra virtual).

Se tiene que:

$$V_{Z_{eq2}} = V_o$$

$$I_f \cdot Z_{eq2} = V_o$$

$$-I_i \cdot Z_{eq2} = V_o$$

$$-\frac{V_i}{Z_{eq1}} \cdot Z_{eq2} = V_o$$

$$\frac{V_o}{V_i} = -\frac{Z_{eq2}}{Z_{eq1}} = H(s)$$

→